

IS-201-Islamic & Pakistan Studies

Fall 2022, Session 2019 (7th Semester)

Mid-Term Exams

Time Allowed: 60 Minutes
Total Marks: 30

- All the related parts of a question must be solved together.
- Start solution of every new part on a new page.

Islamic Studies

Islamic Studies			
Q.1		06	PLO8 CLO1
	Discuss the advices of Hazrat Luqman to his son and its effects in character building.		
Q.2	A	03	PLO8 CLO1
	Translate the following verse. ﴿وَمِنَ النَّاسِ مَنْ يُشْرِكُ لَهُوَ الْحَدِيثُ لَيُضْلِلُ عَنْ سَبِيلِ اللَّهِ بِغَيْرِ عِلْمٍ وَيَتَخَذَهَا هُرُواً أُولَئِكَ لَهُمْ عَذَابٌ مُهِينٌ ۝ وَإِذَا تُشَأِ عَلَيْهِ عَاتِيَنَا وَلَيُمْسِكُنَا كَانَ لَمْ يَتَسْعَهَا كَانَ فِي أَذْيَهٖ وَقَرًا قَبِيزَةٌ بَعْدَابٌ أَلِيمٌ ۝ إِنَّ الَّذِينَ ءَامَنُوا وَعَبَلُوا الصِّلَاحَتِ لَهُمْ جَنَّتُ الْعَصِيمِ ۝﴾		
	B	03	
	And discuss Lah wul Hadith in the light of Quran and Sunnah.		
Q.3	A	03	PLO8 CLO1
	Translate the following Hadith أَنْظُرُوهُمْ إِلَى مَنْ هُوَ أَسْفَلُ مِنْكُمْ، وَلَا تَنْظُرُوهُمْ إِلَى مَنْ هُوَ فَوْقُكُمْ، فَهُوَ أَجْدَرُ أَنْ لَا تُنْزِدُوهُمْ نِعْمَةَ اللَّهِ عَلَيْكُمْ		
	B	03	PLO8 CLO1
	Discuss the golden principle of leading a peaceful life in the light of this Hadith.		

Pakistan Studies

Pakistan Studies			
Q.4		06	PLO 12 CLO3
	Write in detail role of women in Pakistan movement.		
Q.5	Write in detail Features of Objective Resolutions 1949.	06	PPO12 CLO3

EE454 Power System Protection

Mid Term Exam (3 Nov. 2022, Session 2019)

- Start solution of every new question on a new page.
- All the related parts of a question must be solved together.

Time Allowed: 60 Minutes
Total Marks: 30

Q.1	<p>For the portion of power system given in the figure, <i>carry out</i> calculations for the appropriate settings of the protection relays R_b and R_{ab}. Assume available pickup settings to be 4,6,8,10 and 12A. Note that R_{ab} has to act as a backup protection for R_b, while also giving primary protection to its own section AB. On the other hand, you may assume that R_b does not have to be coordinated with any downstream relay. Use the mentioned CT ratios in your calculations. The maximum load current is 100A.</p> <p>Both R_{ab} and R_b are inverse time-delay overcurrent relays, for which the characteristic graph is being provided here.</p>	<p>Min. Fault = 1000 A. Max. Fault = 3000 A. 800 A. 2000 A. 600 A. 1000 A.</p> <p>Time in Seconds Multiples of Relay Tap Setting Time Dial Setting</p>	14	CLO1
Q.2	<p>Briefly mention the <i>application</i> of the following concepts for power system relaying:</p> <ol style="list-style-type: none"> 'Ratio correction factor' for Current Transformers 'Security' for power system protection design 		6	
Q.3	<p>With reference to the portion of power transmission system shown in the accompanying figure (with line impedances shown in parenthesis), evaluate i.e. assess each of the following settings for the distance relay R-AB, via appropriate calculations. (Marks will be for these calculations).</p> <p>Note that the CT ratio for the relay is 500:5 and the PT ratio is 13.86kV:69.3V. Also, for the present numerical problem, ignore overlapping of any zone of R-AB with that of the downstream relays R-BC or R-BD.</p> <p>Zone-1 setting of relay R-AB = $2.6+j26$ Zone-2 setting of relay R-AB = $6+j60$ Zone-3 setting of relay R-AB = $10.5+j10$</p>	10	CLO2	

EE456 Smart Grid


Fall 2022, Session 2019 (07th Semester)
Mid-Term Exams

- All the related parts of a question must be solved together.
- Start solution of every new part on a new page.

Time Allowed: 60 Minutes

Total Marks: 30

Q.1	A	<p>A company in Australian village decided to develop communication infrastructure for smart grid system within some limitations for setup according to main supervision. For HAN network the main requirement is low power consumption and wireless. For NAN network within village ranges between 30 to 50 Km, and the main requirement is wireless communication system.</p> <p>Describe which communication topology will be most suitable according to limitation and requirement for both HAN and NAN respectively? (Just name)</p> <p>Also Explain working of Phasor Measurement Unit that they want to install for NAN communication system?</p>	05	CLO1, Level 2, Understand	PLO1
Q.2	B	<p>Describe the main configuration of Logic Link Control (LLC) that the company want to install for communication system for within grid station?</p>	05	CLO3, Level 4, Analyze	PLO2
	A	<p>Construct the flow chart of Incremental Conductance method and outline different rules for construction of algorithm?</p>	03		
	B	<p>A PV array is connected to boost converter through MPPT Technique whose output is 400 V, while solar irradiance decreased to 500 W/m^2 the voltage of converter decreases up to 160 V. As MPPT Technique is continuously changing the duty cycle then analyze the reason which cause the voltage to decrease?</p>	02		
	C	<p>A Cuk converter has an input of 12 V and is to have an output of -18 V supplying a 40 W load. Select the duty ratio, the switching frequency (50 kHz), the inductor sizes such that the change in inductor currents is no more than 10 percent of the average inductor current, outline the value of inductors and their current waveform?</p>	05		

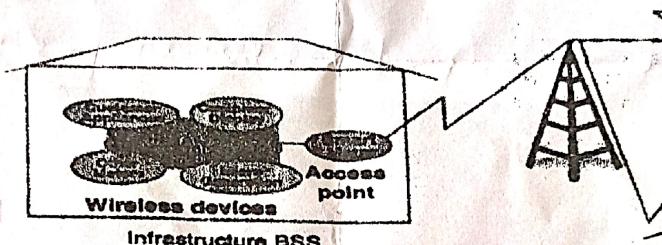


Student Name:

Reg. No.

For the Cuk converter shown, below, draw and outline the currents of switch and capacitor I_{sw} and I_{C1} in timing relation with the switching function.

02

D

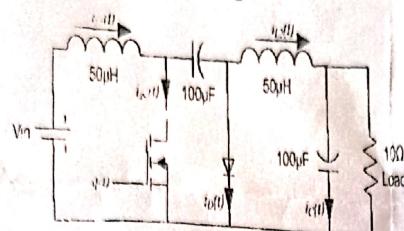

E

- In three phase inverter you are to synthesize a three-phase voltage vector $v_{abc} = [-250 \ 200 \ 50]^t$. Convert this voltage in d-q frame of reference v_x and analyze it.
- Using space vector PWM calculate t_a , t_b and t_o .
- Assume the switching interval is 100 μs. exactly identify the inverter states corresponding to those computed time intervals by drawing the inverter switch states corresponding time interval T_0 , T_1 and T_2 in sector 4 $[V_{011}, V_{001}]$

08

$$t_a = U \left[\cos \alpha - \frac{1}{\sqrt{3}} \sin \alpha \right]$$

$$V_a = \frac{2}{\sqrt{3}} \cdot V_x \cdot \sin \left(\frac{\pi}{3} - \alpha \right)$$

$$T_{abc-dq} = \sqrt{3} \begin{bmatrix} 1 & -\frac{1}{2} & -\frac{1}{2} \\ 0 & \frac{\sqrt{3}}{2} & -\frac{\sqrt{3}}{2} \end{bmatrix}$$

$$t_b = \frac{2}{\sqrt{3}} \cdot U \cdot \sin \alpha$$

$$V_b = \frac{2}{\sqrt{3}} \cdot V_x \cdot \sin \alpha$$

CLO3, Level 4, Analyze

PLO2



length = 60eV